

EE2-08C Numerical Analysis

Group 9

Exercise 1

This simple RL circuit forms a high pass filter circuit which takes an input signal V_{in} and only allows the high frequency components to pass. Despite the inductor being less convenient than a capacitor, this RL circuit can approach the model of a DC motor. In this specific case, we want to model a DC motor with inertia $250 \mu\text{sNm/s}^2$ and $T_{max} = 50\text{mNm/A}$. To do so, according to KCL, we know that

$$V_{in}(t) = v_L(t) + v_R(t)$$

and therefore:

$$V_{in}(t) = L \frac{d}{dt} i_L(t) + R i_L(t)$$

$i_L(t)$ is the state that we will solve following the three different second-order Runge Kutta methods. All methods follow the same pattern:

$$x_{i+1} = x_i + h$$

h being the step size and

$$y_{i+1} = y_i + h(ak_1 + bk_2)$$

where

$$k_1 = f(x_i, y_i)$$

$$k_2 = f(x_i + ph, y_i + qk_1h)$$

and the values of a, b, p and q depend on which method we are using:

Parameter	Heuns	Midpoint	Ralston
a	1/2	0	1/4
b	1/2	1	3/4
p	1	1/2	2/3
q	1	1/2	2/3

Each method will approximate the exact solution according to these parameters. Therefore, the smaller the step size h , the more exact the method will approximate the solution. After doing so, the output value will be obtained as follows:

$$V_{out} = V_{in}(t) - R i_L(t)$$

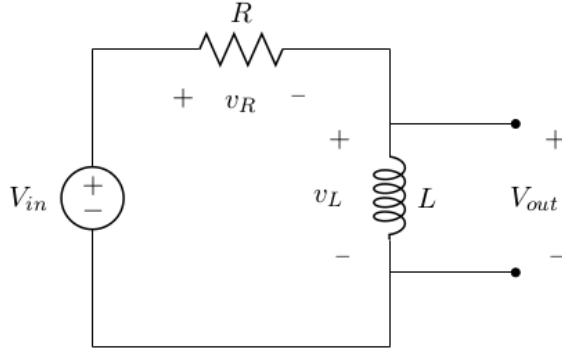


Figure 1: RL Circuit