

EE2-08C Numerical Analysis

Group 9

Exercise 1

The Problem

Exercise 2

The Problem

Exercise 3

The Problem

Exercise 4

The Problem

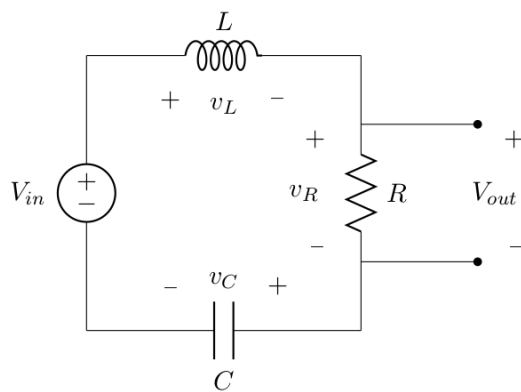


Figure 1: RLC Circuit